

## SYNCHRONOUS-UP-COUNTER

### AIM:

To implement 4 bit synchronous up counter and validate functionality.


### SOFTWARE REQUIRED:

Quartus prime


### THEORY
 
#### 4 bit synchronous UP Counter

If we enable each J-K flip-flop to toggle based on whether or not all preceding flip-flop outputs (Q) are "high," we can obtain the same counting sequence as the asynchronous circuit without the ripple effect, since each flip-flop in this circuit will be clocked at exactly the same time:



A four-bit synchronous "up" counter

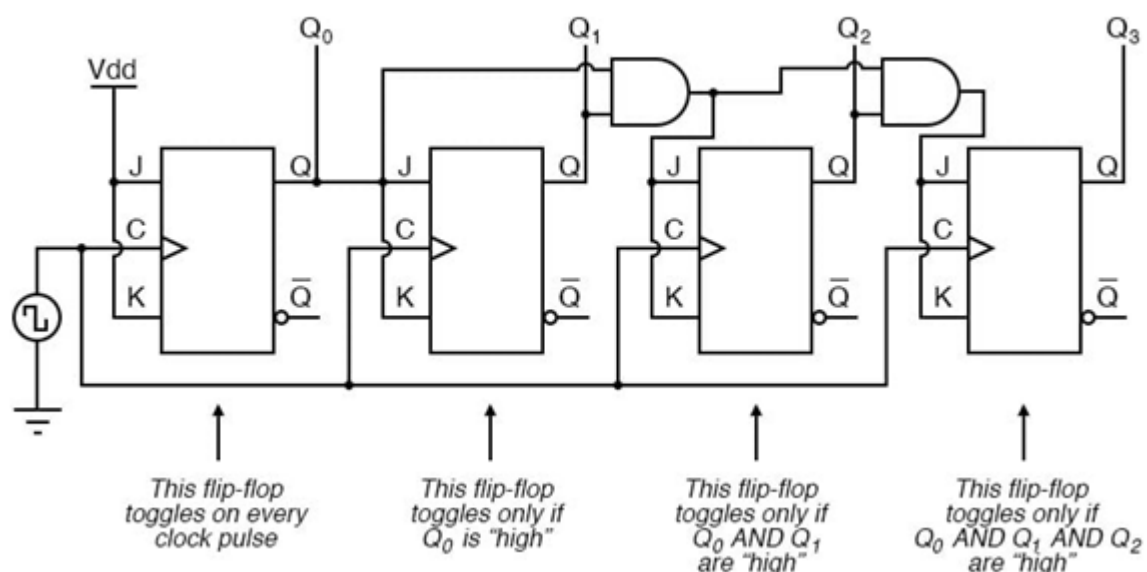

Each flip-flop in this circuit will be clocked at exactly the same time. The result is a four-bit synchronous "up" counter. Each of the higher-order flip-flops are made ready to toggle (both J and K inputs "high") if the Q outputs of all previous flip-flops are

"high." Otherwise, the J and K inputs for that flip-flop will both be "low," placing it into the "latch" mode where it will maintain its present output state at the next clock pulse. Since the first (LSB) flip-flop needs to toggle at every clock pulse, its J and K inputs are connected to Vcc or Vdd, where they will be "high" all the time. The next flip-flop need only "recognize" that the first flip-flop's Q output is high to be made ready to toggle, so no AND gate is needed. However, the remaining flip-flops should be made ready to toggle only when all lower-order output bits are "high," thus the need for AND gates.

### Procedure

- 1.Type the program in Quartus software.
- 2.Compile and run the program.
- 3.Generate the RTL schematic and save the logic diagram.
- 4.Create nodes for inputs and outputs to generate the timing diagram.
- 5.For different input combinations generate the timing diagram.

### PROGRAM

/\* Program for flipflops and verify its truth table in quartus using Verilog programming.

```
module deproj11(out,clk,rst);  
input clk,rst;  
output reg [3:0]out;  
always @ (posedge clk)  
begin  
    if(rst)  
        out<=0;  
    else  
        out <= out+1;  
    end  
end  
endmodule
```

Developed by:


AKASH M

RegisterNumber:


24900103

\*/

### RTL LOGIC UP COUNTER

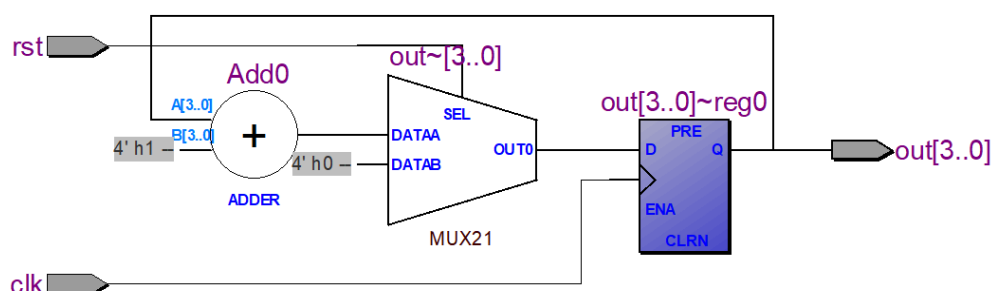

# TIMING DIAGRAM FOR IP COUNTER

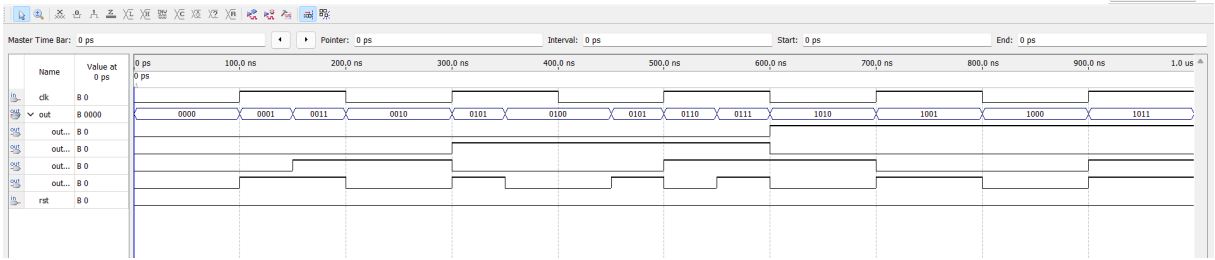

## RESULTS

Thus, the JK Flip-Flop is designed, and its functionality is validated using truth table and timing diagrams

